

ASSIGNMENT – 1

BUILD A SMART HOME IN THINKERCAD

Assignment date	26 September 2022
Student Name	DHARMARAJ E
Student Roll Number	815119106010
Maximum Marks	2 Marks


QUESTION -1:

Build a smart home in thinkercad

Use atleast 2 sensor, led, buzzer in a circuit. Stimulate in a single code.

Solution:

CIRCUIT :

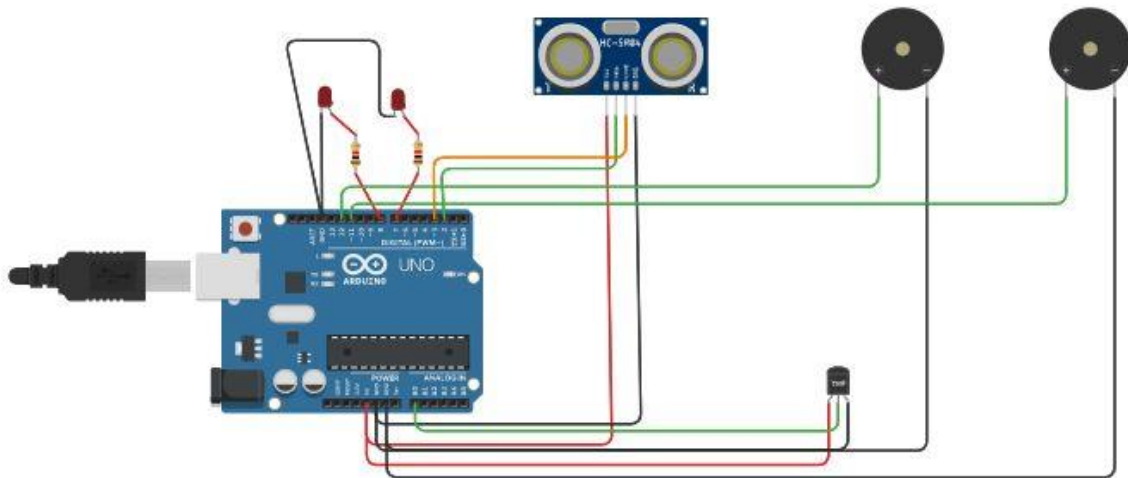

CODE :

```
int
t=2;

int e=3;
void setup()
{
  Serial.begin(9600);
  pinMode(t,OUTPUT);
  pinMode(e,INPUT);
  pinMode(12,OUTPUT);
}
void loop()
{
  //ultrasonic sensor
  digitalWrite(t,LOW);
  digitalWrite(t,HIGH);
  delayMicroseconds(10);
  digitalWrite(t,LOW);
  float dur=pulseIn(e,HIGH);
  float dis=(dur*0.0343)/2;
  Serial.print("Distance is: ");
  Serial.println(dis);

  //LED ON
  if(dis>=100)
  {
    digitalWrite(8,HIGH);
    digitalWrite(7,HIGH);
  }

  //Buzzer For ultrasonic Sensor
  if(dis>=100)
  {
    for(int i=0; i<=30000; i=i+10)
    {
      tone(12,i);
      delay(1000);
      noTone(12);
      delay(1000);
    }
  }
}
```

```

}

//Temperate Sensor
double a= analogRead(A0);
double t=((a/1024)*5)-0.5)*100;
Serial.print("Temp Value: ");
Serial.println(t);
delay(1000);

//LED ON
if(t>=100)
{
    digitalWrite(8,HIGH);
    digitalWrite(7,HIGH);
}

//Buzzer for Temperature Sensor
if(t>=100)
{
    for(int i=0; i<=30000; i=i+10)
    {
        tone(12,i);
        delay(1000);
        noTone(12);
        delay(1000);
    }
}

//LED OFF
if(t<100)
{
    digitalWrite(8,LOW);
    digitalWrite(7,LOW);
}
}

```