ASSIGNMENT - 1

BUILD A SMART HOME IN THINKERCAD

Assignment date	26 September 2022
Student Name	MADHAN DEEPAK R
Student Roll Number	815119106020
Maximum Marks	2 Marks


QUESTION -1:

Build a smart home in thinkercad

Use atleast 2 sensor, led, buzzer in a circuit. Stimulate in a single code.

Solution:

CIRCUIT:

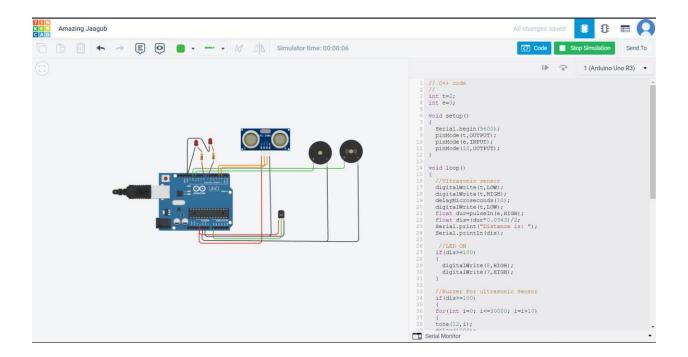

CODE:

```
C++
code
       //
       int t=2;
       int e=3;
       void setup()
         Serial.begin(9600);
         pinMode(t,OUTPUT);
         pinMode(e,INPUT);
         pinMode(12,OUTPUT);
       }
       void loop()
         //Ultrasonic sensor
         digitalWrite(t,LOW);
         digitalWrite(t,HIGH);
         delayMicroseconds(10);
         digitalWrite(t,LOW);
         float dur=pulseIn(e,HIGH);
         float dis=(dur*0.0343)/2;
         Serial.print("Distance is: ");
         Serial.println(dis);
          //LED ON
         if(dis>=100)
         {
           digitalWrite(8,HIGH);
           digitalWrite(7,HIGH);
         }
         //Buzzer For ultrasonic Sensor
         if(dis>=100)
         for(int i=0; i<=30000; i=i+10)
         tone(12,i);
         delay(1000);
         noTone(12);
         delay(1000);
         }
         }
```

```
//Temperate Sensor
  double a= analogRead(A0);
  double t=(((a/1024)*5)-0.5)*100;
  Serial.print("Temp Value: ");
  Serial.println(t);
  delay(1000);
 //LED ON
  if(t>=100)
   digitalWrite(8,HIGH);
    digitalWrite(7,HIGH);
 }
 //Buzzer for Temperature Sensor
  if(t>=100)
  for(int i=0; i<=30000; i=i+10)
 tone(12,i);
 delay(1000);
  noTone(12);
  delay(1000);
 }
  //LED OFF
  if(t<100)
    digitalWrite(8,LOW);
    digitalWrite(7,LOW);
 }
}
```